
 
 





CPU – principles of operation

- ▶ CPU and similar chips mostly use CMOS technology (1963)
 - ▶ C=Complementary – both polarities of transistors available
 - A mix of n-type and p-type transistors on the same chip
 - The mix allows control of both incoming and outgoing current at a gate
 - ▶ MOS=Metal-Oxide-Semiconductor – a particular transistor technology (1959)
 - A kind of FET=Field-Effect-Transistor – a transistor controlled by voltage on "Gate"
 - Behaviorally similar to a triode vacuum tube (1908) but much smaller voltage, size, price
 - Also called Unipolar – only one kind of current-carriers used (in one transistor)
 - n-type transistors use electrons, p-type use holes
 - The first transistors (1947) were Bipolar (both electrons and holes used to transport current) and controlled by current – no longer used in computing after ~1980
 - ▶ DRAM (1968) and Flash (1980) chips use slightly different technologies
 - the memory effect is provided by a specially constructed transistor
 - usually not mixable with CPU in the same chip
 - only low-density devices like embedded CPUs can mix CMOS logic and Flash

 

► Four transistors constitute a **NAND** gate

   
- Two inputs: A, B
- Output = $\!(A\&\&B)$
- High voltage on both inputs closes the p-type transistors (current sources, top) and opens the n-type transistors (current sink, bottom)



► Power consumption

- Gates and wires connected to Out form a capacitor which must be charged and discharged in each cycle – proportional to frequency, reduced by Dennard scaling
- Short-circuit current (all transistors are open during state changes)
- Leakage through closed transistors – increased by geometry scaling down

Full 1-bit adder

 


► Full adder = 1-bit addition with carry in and carry out

► The sum of three 0/1 inputs may be 0/1/2/3 – representable by 2-bit output

$$(Co \ll 1) | S = A + B + Ci$$

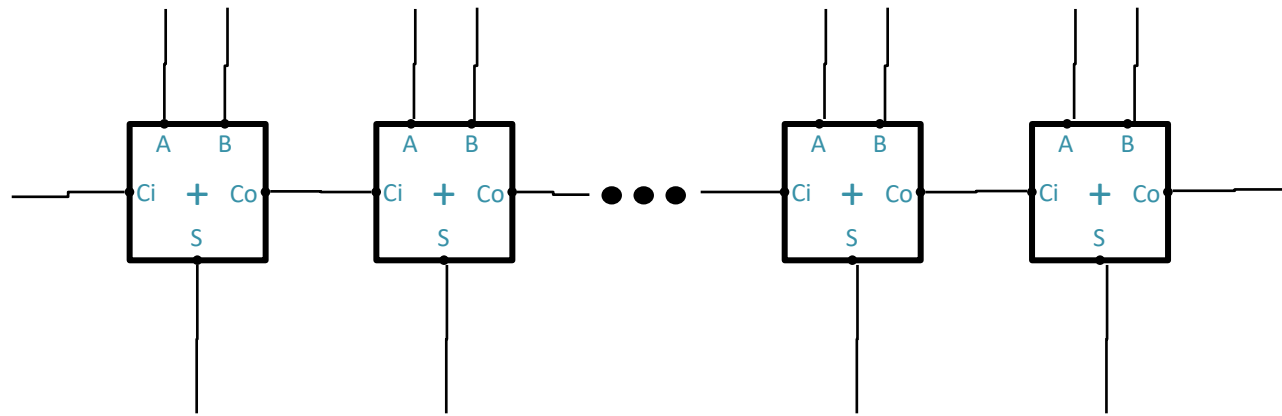
► The circuit is made smaller with three-input NAND and NOR gates



► N-bit addition with carry in and carry out

- $O(N)$ delay - too slow for large N
- Recursive “dynamic-programming” construction used for large N
 - $O(\log N)$ delay, but significantly more gates needed


Combinational vs. sequential circuits

 

- ▶ **Combinational** circuit = directed acyclic graph = state-less circuit
 - ▶ The signal is only delayed, proportionally to the longest path length
- ▶ **Sequential** circuit = cyclic graph
 - ▶ Cycles cause state-full behavior (usually through positive feed-back)
 - ▶ Various kinds of registers
 - “Register” is originally a digital-design term – any state-full circuit used to store information
 - The simplest case of register is the 1-bit Set/Reset Latch depicted above
 - A *CPU register* (as referenced in machine code) is, in digital-design terminology, a part of small *Static RAM*
 - *Static RAM* is an *addressable* array of n-bit registers – one of them is activated by a *binary decoder* (a combinational circuit)
 - ▶ More sophisticated cases (e.g. clock dividers)

- ▶ **Process (lithography)** – the technology of the chip-producing *foundry (fab)*
 - ▶ Often simply denoted by geometric resolution in nanometers
 - ▶ Decides the geometrical, electrical, and timing properties of transistors
- ▶ **Physical design** – produces *masks* for manufacturing
- ▶ **Transistor Level** – network of transistors (and other elements)
 - ▶ Often skipped as each gate type has its optimized physical design
- ▶ **Logic (Gate) Level** – network of gates, latches, etc.
- ▶ **RTL (Register-Transfer Level) design**
 - ▶ Circuits limited to Combinational circuits + Registers
 - Registers controlled by a common clock
 - ▶ Originally a principle of systematic (but not optimal) gate-level design
 - ▶ Later an intermediate level of design, specified as program-like text (not schematically)
 - ▶ Now usually generated from system-level design
- ▶ **System Level design**
 - ▶ Done in **System-C**, **Verilog** (1986), or **VHDL** (1981)
 - Effectively parallel-programming languages
 - Verilog and VHDL also allow direct RTL/Logic/Transistor-level design, analog and simulation models
 - There is probably more work done than in gcc/clang/msvc/javac together
 - Restrictions (w.r.t. general programming) allow transformation to RTL designs
 - The transformation shares some algorithms with parallelizing compilers
- ▶ **Electronic Design Automation (EDA) software is a 10-billion USD/year industry**
 - ▶ The largest player is Synopsys, Inc. (market cap USD 35B, cf. Microsoft 1700B)


Combinational vs. sequential N-bit adder

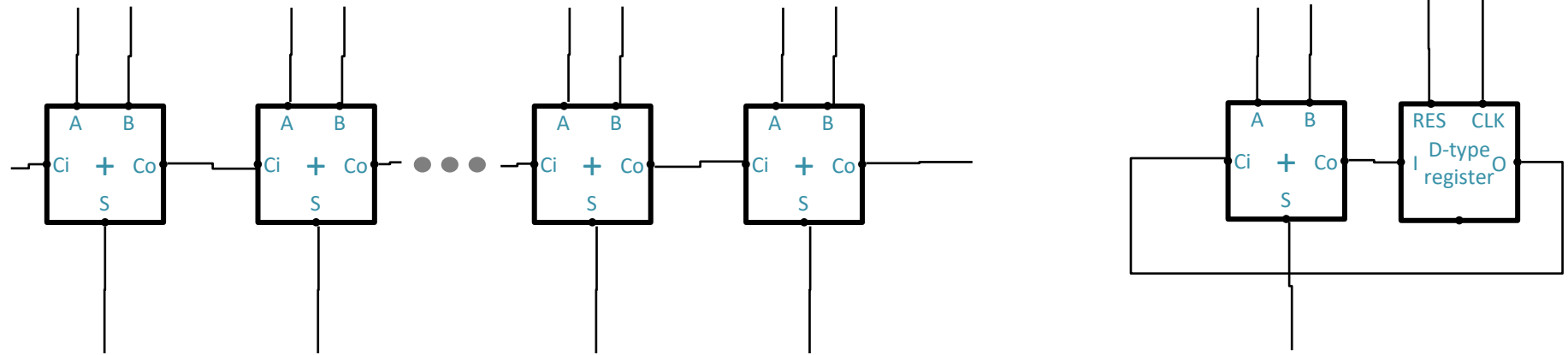

▶ Sequential N-bit adder

- ▶ Input bits serialized on 2 wires, synchronized, in LSB-to-MSB order
- ▶ Requires clock to sample inputs and to control the (D-type) register
 - Due to delay, outputs (Co, S) must be sampled later, at the end of clock cycle
- ▶ Slower even than naïve combinational but $O(1)$ gates

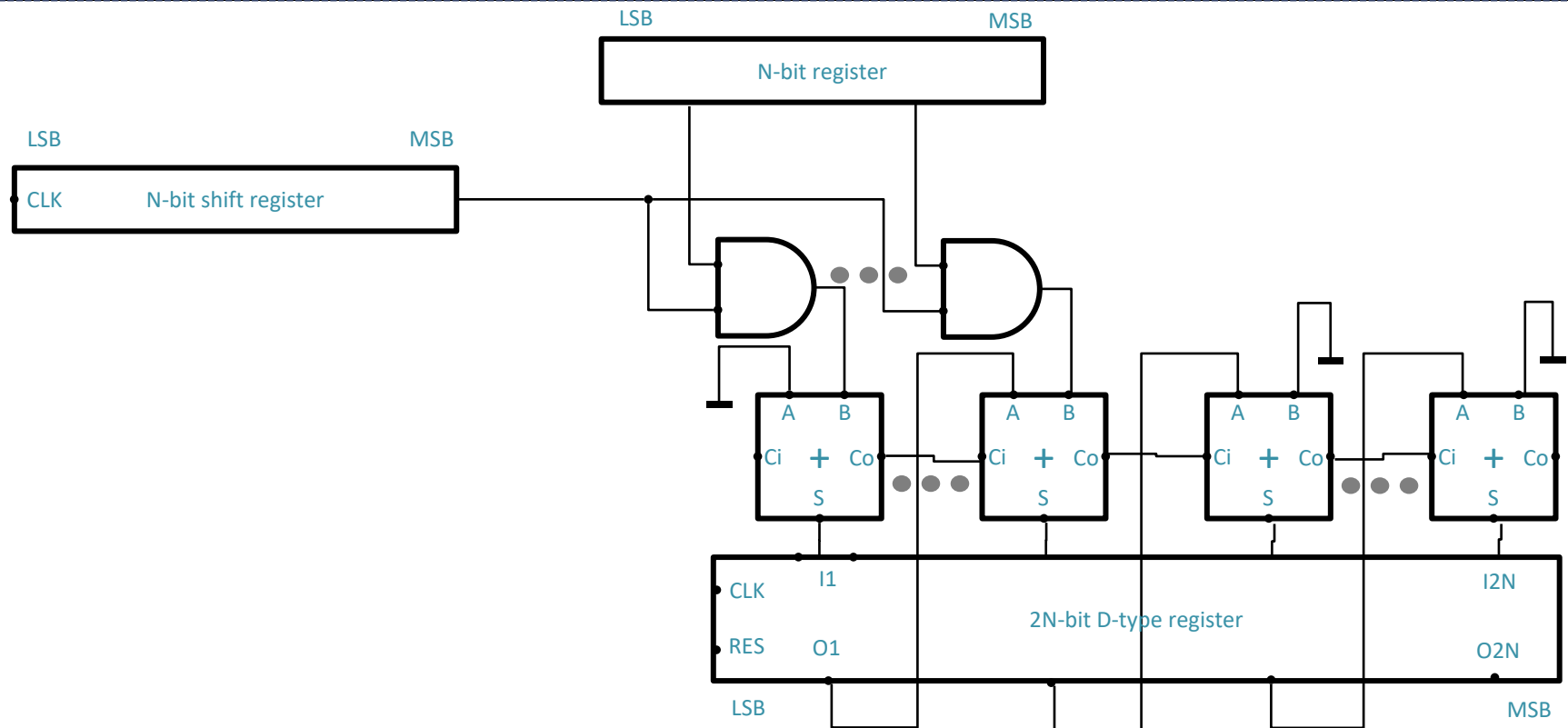
Sequential $N \times N$ -to- $2N$ -bit multiplier



▶ The school multiplication algorithm in binary digits


- ▶ Shown mirrored wrt. school convention, i.e. with LSB on the left and MSB on the right
- ▶ One operand fixed, one being shifted by a shift register
- ▶ $1 \times N$ -bit multiplication implemented by N AND gates
- ▶ Addition of N N -bit results implemented by $2N$ full adders with shifting loopback
- ▶ Total delay $O(N \times N)$; may be improved to $O(N \times \log N)$ with optimized $2N$ -bit adder

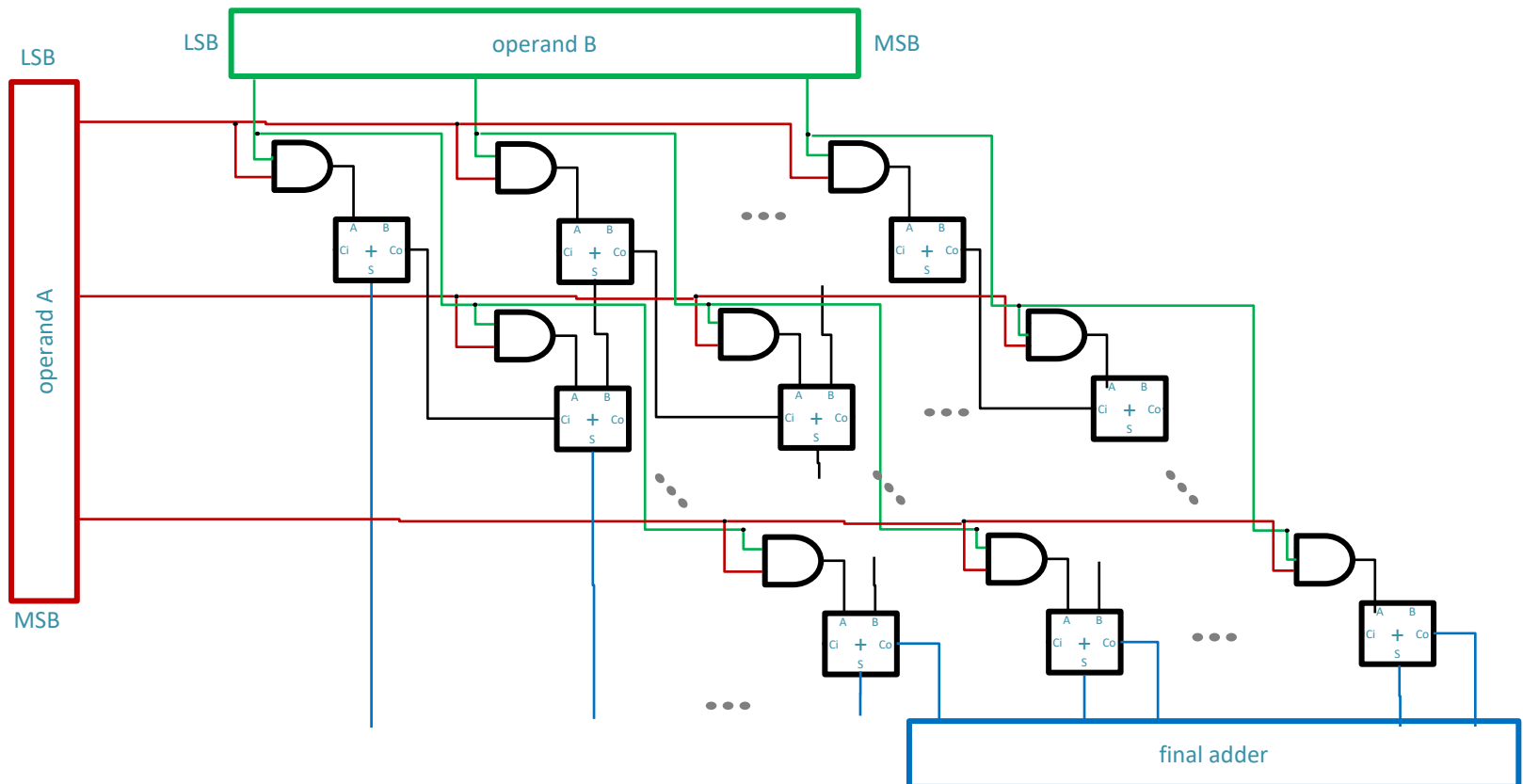Combinational $N \times N$ -to- $2N$ -bit multiplier




- ▶ The school multiplication algorithm in binary digits
 - ▶ Shown mirrored wrt. school convention, i.e. with LSB on the left and MSB on the right
 - ▶ $1 \times N$ -bit multiplication implemented by $N \times N$ AND gates
 - ▶ Addition of N N -bit results implemented by $N \times N$ full adders, then by a final $N+N$ -bit adder
 - ▶ Total delay $O(N)$
 - In real designs (1992), reduced to half by radix-4 Booth encoding of operands

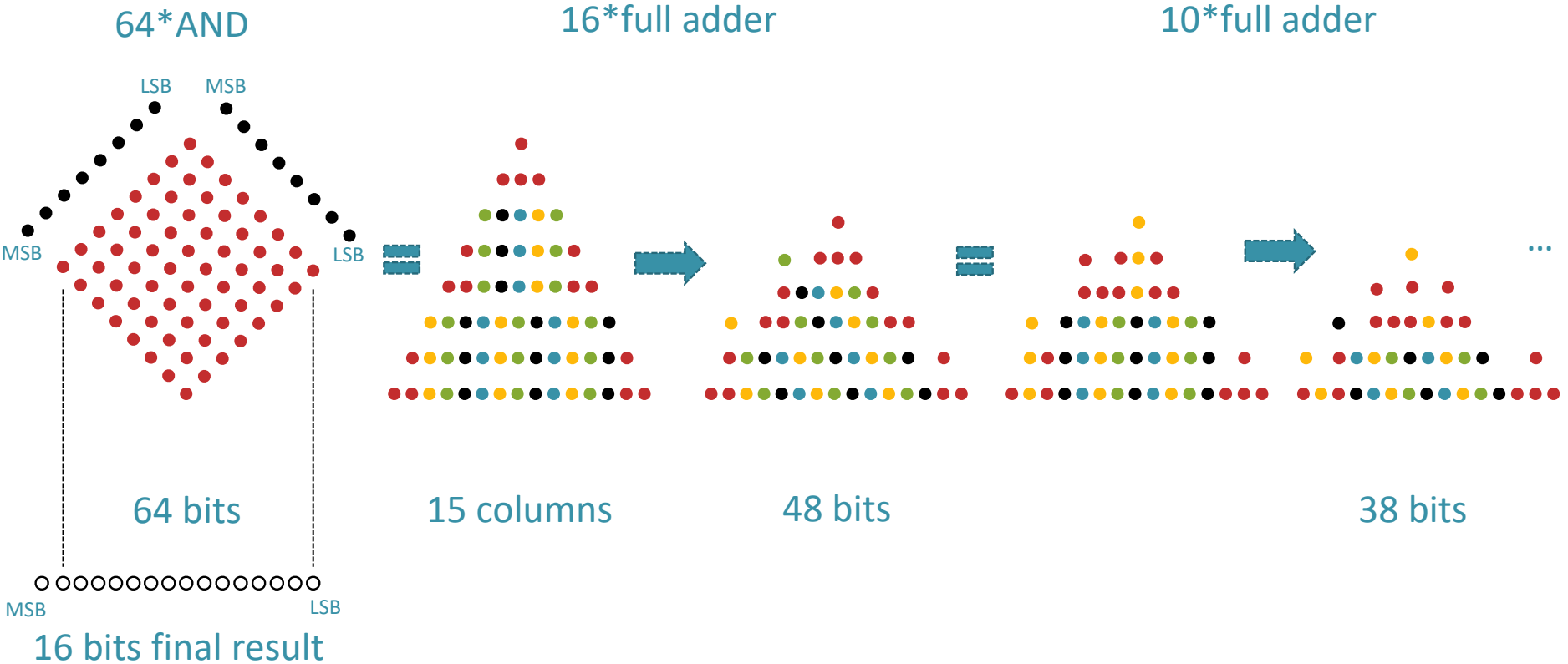Wallace-tree multiplier (invented 1964, used after 2000)



- ▶ 1-bit multiplier = AND gate
- ▶ N-bit multiplier must add $N*N$ 1-bit results, properly shifted
 - ▶ Wallace-tree: Instead of adding bits in the columns, recursively reduce number of operands by full adders
 - A full adder converts three bits (in the same column) into two bits (in two adjacent columns)
 - Each layer reduces the number of bits in a column from M to $(M/3)+(M\%3)$ but sends $(M/3)$ bits to the left
 - After $O(\log_{3/2} N*N) = O(\log N)$ layers, the remaining small columns are summed by optimized $2N$ -bit adder
 - This algorithm is done in the circuit generator – the generated circuit is combinational with $O(\log N)$ delay

Wallace-tree multiplier staged

 

- ▶ The Wallace-tree consists of tens of layers ($\log_{1.22} 64 = 21$)
 - Each layer is a set of independent full adders
- ▶ The total delay may be longer than the desired system clock period
- ▶ Registers inserted after each K layers, delay between registers less than a clock
- ▶ A new multiplication may be started in each clock period = **pipelining**

Arithmetic units in general

- ▶ **Sequential implementation**
 - Hardware equivalent of loop in a program
- ▶ The same hardware used repeatedly during the same operation
- ▶ **Minimum number of transistors**, large latency
 - The registers incur additional delay
- ▶ **Purely combinational implementation**
 - Hardware equivalent of mathematical formula
- ▶ Each piece of hardware used only once during the same operation
 - Idle for most of the time
- ▶ Large number of transistors, **minimum latency**
- ▶ Advanced (non-iterative) algorithms possible (e.g. Wallace multiplier)
- ▶ **Staged combinational implementation**
 - Hardware equivalent of unrolled loop (but iterations may differ)
- ▶ Each piece of hardware used once during a clock period
 - May be used for another operation in the next period
- ▶ Even larger number of transistors, latency similar to sequential implementation
 - Latency may be lower if a stage corresponds to more iterations of the algorithm
- ▶ **Large throughput** due to pipelining

Arithmetic units in general

- ▶ When increasing transistor speed is no longer possible (2005)...
- ▶ ... there are two ways to improve throughput:
 - ▶ Replace sequential by staged combinational implementation
 - Allows **pipelining**
 - ▶ Implement more than one arithmetic unit
 - Multiple units in the same pipeline (SIMD instructions)
 - A SIMD instruction may also use two pipelines in parallel
 - Multiple pipelines (processing instructions of the same thread)
 - Hyperthreading: More than one thread shares the same set of pipelines
 - Multiple cores/sockets (processing instructions of different threads)
- ▶ The price:
 - ▶ Increased number of transistors
 - ▶ Increased complexity of synchronization (additional energy consumption)
- ▶ Throughput (number of operations per time) is improved
- ▶ Latency (time required to finish an operation) is NOT improved
 - ▶ Latency may be improved by advanced circuit designs

Arithmetic units in general

- ▶ The reality in Intel/AMD CPUs (2010 to 2020):
 - ▶ Integer addition/subtraction is single-clock (unstaged combinational)
 - FP addition/subtraction usually 3 clocks due to shifting/normalization, pipelined
 - ▶ Multiplication is staged combinational
 - Latency usually 3 to 5 clocks
 - Pipelined: Throughput 1 instruction per clock per pipeline
 - ▶ Division is always iterative (sequential)
 - Latency 20 to 80 clocks (FP often faster than integer)
 - Latency may depend on actual values
 - The pipeline is blocked – very small throughput
 - ▶ Bit operations (AND/OR/XOR) are single-clock
 - Shifts/rotations may cost more than one clock
 - In terms of chip layout, ALUs are rather wide (across bits) than deep (across stages)
 - Any information travelling across (many) bits is problematic
 - ▶ SIMD operations: usually the same latency as their scalar counterpart
 - Only few iterative operations (FDIV) available in the SIMD instruction set
 - Some wide-vector instructions implemented as two half-width operations pipelined
 - This fact heavily influenced the SIMD instruction set